

Error Detection for Borrow-Save Adders Dedicated to ECC Unit

Julien Francq, Jean-Baptiste Rigaud, Pascal Manet, Assia Tria,
Arnaud Tisserand



August 10, 2008

Part 1

Introduction

Elliptic Curves

- **Definition.** An elliptic curve over a finite field \mathbb{F}_p (with p prime) is the set of points $(x, y) \in E$

$$E : y^2 = x^3 + ax + b \cup \{\infty\}$$

- **Fact.** $E(\mathbb{F}_p)$: **additive group**
 - Neutral element: ∞
 - Group operation: **addition (\oplus)** [“chord-and-tangent” law]
- **Addition formulæ.** Let $P_1 = (x_1, y_1)$ and $P_2 = (x_2, y_2)$, $P_1 \oplus P_2 = (x_3, y_3)$ where

$$x_3 = \lambda^2 - x_1 - x_2 \text{ and } y_3 = (x_1 - x_3)\lambda - y_1$$

$$\text{with } \lambda = \begin{cases} \frac{y_2 - y_1}{x_2 - x_1}, & \text{if } P_1 \neq \pm P_2 \text{ [Addition]} \\ \frac{3x_1^2 + a}{2y_1}, & \text{if } P_1 = P_2 \text{ [Doubling]} \end{cases}$$

Elliptic Curve Cryptography (ECC)

- [Miller, CRYPTO 1986], [Koblitz, MC, 1987]

Elliptic Curve Discrete Logarithm Problem (ECDLP)

Let $\mathbb{G} = \langle P \rangle = \{\infty, P, [2]P, \dots, [n-1]P\} \subseteq E(\mathbb{F}_p)$,
with $n = \text{ord}_E(P)$ prime.

Given points $P, Q \in \mathbb{G}$, compute d such that

$$Q = [d]P = \underbrace{P \oplus P \oplus \dots \oplus P}_{d \text{ times}}$$

- **ECDLP is intractable** if elliptic curve parameters (p, E, P, n) are carefully chosen.
- **RSA-1024 \simeq ECC-160**

Fault Attacks and Countermeasures

- Attacks on ECC
 - Side-channel attacks
 - **Fault attacks** [$E \rightarrow \hat{E}$, where $n' = \text{ord}_{\hat{E}}(P/\hat{P}) < n$]
- Standard countermeasures for fault attacks protect $Q = [d]P$
- \rightarrow **Modular arithmetic's layer** must be also protected...
- ...by using **parity-preserving logic gates!**
- Outline:

Fault Attacks and Countermeasures

- Attacks on ECC
 - Side-channel attacks
 - **Fault attacks** [$E \rightarrow \hat{E}$, where $n' = \text{ord}_{\hat{E}}(P/\hat{P}) < n$]
- Standard countermeasures for fault attacks protect $Q = [d]P$
- \rightarrow **Modular arithmetic's layer** must be also protected...
- ...by using **parity-preserving logic gates!**
- Outline:
 - Parity-Preserving Logic Gates (PPLGs)

Fault Attacks and Countermeasures

- Attacks on ECC
 - Side-channel attacks
 - **Fault attacks** [$E \rightarrow \hat{E}$, where $n' = \text{ord}_{\hat{E}}(P/\hat{P}) < n$]
- Standard countermeasures for fault attacks protect $Q = [d]P$
- \rightarrow **Modular arithmetic's layer** must be also protected...
- ...by using **parity-preserving logic gates!**
- Outline:
 - Parity-Preserving Logic Gates (PPLGs)
 - Implementing parity-preserving logic circuits

Fault Attacks and Countermeasures



- Attacks on ECC
 - Side-channel attacks
 - **Fault attacks** [$E \rightarrow \hat{E}$, where $n' = \text{ord}_{\hat{E}}(P/\hat{P}) < n$]
- Standard countermeasures for fault attacks protect $Q = [d]P$
- \rightarrow **Modular arithmetic's layer** must be also protected...
- ...by using **parity-preserving logic gates!**
- Outline:
 - Parity-Preserving Logic Gates (PPLGs)
 - Implementing parity-preserving logic circuits
 - Implementation results

Part 2

PPLGs

PPLGs

  - [Fredkin *et al.*, TP, 1982], [Feynman, ON, 1985], [Parhami, ACSSC 2006]
- Feynman double-gate (F2G), Fredkin gate (FRG)



Implementing Parity-Preserving Logic Circuits

Implementation Results

Conclusion


Part 3

Implementing Parity-Preserving Logic Circuits

Why Borrow-Save for Modular Arithmetic?


- Compute $Q = [d]P$ efficiently \rightarrow efficient $+/-, \times, x^{-1}$
- \Rightarrow **Addition** must be efficiently implemented!
 - \rightarrow Borrow-Save Addition (BSA) **without carry-propagation**
- $A = (a_{l-1} \cdots a_1 a_0)_{BS}$ where $a_i \in \{-1, 0, 1\}$ are coded on 2 bits a_i^+ and a_i^- such that $a_i = a_i^+ - a_i^-$ and
 
$$A = \sum_{i=0}^{l-1} a_i 2^i = \sum_{i=0}^{l-1} (a_i^+ - a_i^-) 2^i$$



Implementing Parity-Preserving Circuits (1/3)

 - 1. Choose the protected part of the circuit.
 - How many output bits are protected at a time, what is the protection level? / Performance
 - 2 BSA output bits (s_{i+1}^- , s_i^+)
 - 5 BSA input bits are concerned: a_i^+ , b_i^+ , a_i^- , b_i^- , c_i^+




Implementing Parity-Preserving Circuits (2/3)

● 2. Get the corresponding logic equations.

- Sufficiently **simple circuit**

 - 1st row of PPMs $\begin{cases} c_i^- = a_i^+ \oplus b_i^+ \oplus a_i^- \\ c_i^+ = a_{i-1}^+ \cdot b_{i-1}^+ + a_{i-1}^+ \cdot \overline{a_{i-1}^-} + b_{i-1}^+ \cdot \overline{a_{i-1}^-} \end{cases}$
- 2nd row of PPMs $\begin{cases} s_{i+1}^- = c_i^- \cdot b_i^- + c_i^- \cdot c_i^+ + b_i^- \cdot c_i^+ \\ s_i^+ = c_i^- \oplus b_i^- \oplus c_i^+ \end{cases}$



Implementing Parity-Preserving Circuits (3/3)


- **3. Transform the logic equations in Galois field.**

(using $f + g = f \oplus g \oplus f.g$)

- 1st row of PPMs $\left\{ \begin{array}{l} c_i^- = a_i^+ \oplus b_i^+ \oplus a_i^- \\ c_i^+ = a_{i-1}^+ \cdot b_{i-1}^+ \oplus a_{i-1}^+ \cdot \overline{a_{i-1}^-} \oplus b_{i-1}^+ \cdot \overline{a_{i-1}^-} \end{array} \right.$
- 2nd row of PPMs $\left\{ \begin{array}{l} s_{i+1}^- = c_i^- \cdot b_i^- \oplus c_i^- \cdot \overline{c_i^+} \oplus b_i^- \cdot \overline{c_i^+} \\ s_i^+ = c_i^- \oplus b_i^- \oplus c_i^+ \end{array} \right.$


- **4. Implement these equations thanks to PPLGs.**

PPM1 Cell

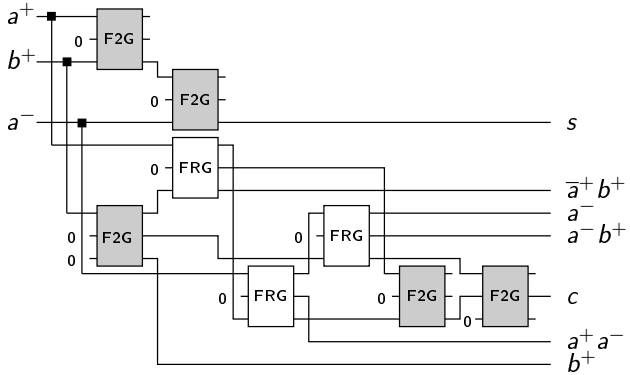


- Triplication: $F2G(a = x, b = 0, c = 0, p = x, q = x, r = x)$
- "Garbage bits"

PPM2 Cell

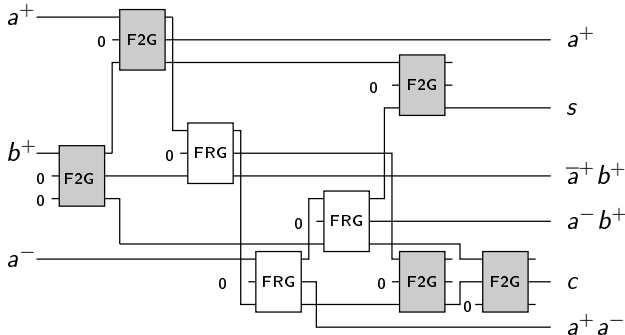

- Triplication: $F2G(a = x, b = 0, c = 0, p = x, q = x, r = x)$
- "Garbage bits"

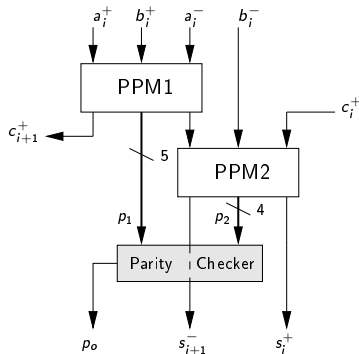Elementary Cell of our Fault-Tolerant BSA



$$p_0 = \beta_1 + \beta_2 + \beta_3$$

$$\text{With: } \beta_1 = a_i^+ \oplus b_i^+ \oplus a_i^- \oplus c_i^-, \beta_2 = a_i^+ \oplus b_i^+ \oplus a_i^- \oplus p_1 \oplus c_{i+1}^+,$$

$$\beta_3 = c_i^+ \oplus b_i^- \oplus c_i^- \oplus p_2 \oplus s_{i+1}^- \oplus s_i^+$$

Part 4

Implementation Results

Performance

Architecture	Area (μm^2)	Latency (ns)
BSA-160 w/o EDC	134,440	1.39
BSA-160 with EDC	698,157	5.69
Overhead	x5.2	x4.1

Architecture	Area (μm^2)	Latency (ns)
ALU-160 w/o EDC	3,096,103	8.38
ALU-160 with EDC	4,270,313	19.96
Overhead	x1.4	x2.4

- ALU mainly consists in 2 BSAs, MUXs, shifts and registers
- Synthesized in C35 CORELIB technology using Design Vision

Evaluation of the Detection Capabilities

Number of faulty bits	1 bit	2 bits
Detected faults	80.0%	86.8%
Unfaulty computations	14.3%	2.1%
Undetected faults	5.7%	11.1%

Part 5

Conclusion and future works

Conclusion and future works

- **Fault-tolerant** elliptic curve cryptoprocessor unit...
- ...using **parity-preserving logic gates**.
- Protecting **only borrow-save adders** implies an acceptable area overhead (+40%)...
- ...but a less acceptable latency overhead (+140%).
- Improvement by using **optimized PPLGs** or **reversible gates** (e.g., Toffoli and Peres gate)
- Protect **control logic**

Affiliation

- ENSM-SE/SGC



- Secure Embedded Systems And Microelectronics team
- LIRMM
 - ARITH team
 - Design of secured arithmetical operators
- Technological Bricks for Reinforcing Security project
 - Partners: CEA-LETI, Gemalto, Smart Packaging Solutions